

CPEN 211 Introduction to Microcomputers, 2024
Lab Proficiency Test #3


Question 1 [2.5 marks, part marks possible]: In a file “q1.sv” write synthesizable Verilog implementing the datapath in the figure below. Your top-level module *must* be declared as:

```
module datapath(clk,Rd,w,in,sel,Ri,Rj,lsb,aop,loadb,out);
    input clk, w, sel, loadb;
    input [1:0] Rd, Ri, Rj;
    input [15:0] in;
    input [1:0] aop;
    output lsb;
    output [15:0] out;
```

Use the signal names as shown in the figure. ALU is combinational logic defined as follows:

aop	ALU Operation
2'b00	aout = iout >> 1
2'b01	aout = iout << 1
2'b10	aout = iout + jout
2'b11	aout = iout

The output aL of the ALU is a 1-bit signal that is 1 when bit 0 of aout is 1 and 0 otherwise. The datapath contains three 16-bit registers with load enable and clock input clk, connected to 16-bit signals R0, R1, and R2. Datapath output out is connected to R2. The block “decoder” is a one hot decoder without 2-bit input Rd and 3-bit output load. The inputs “Ri” and “Rj” are 2-bit binary selects, input “loadb” is a load enable. You can include testbenches in q1.sv. The testbench tb_check_q1 in tb.sv inside <https://cpen211.ece.ubc.ca/2024/lpt3-check-T7wBe9Vz.zip> should print “INTERFACE OK” and generate no ModelSim warnings if your interface is compatible with the autograder (cut and paste link if clicking does not work). Your q1.sv **must** include definitions for any modules instantiated. *Hint:* Tor’s solution for q1.sv is 29 lines. **Upload your Verilog file named “q1.sv” for Question 1 on “Lab Proficiency Test #3” on Canvas before 5:45 pm.**

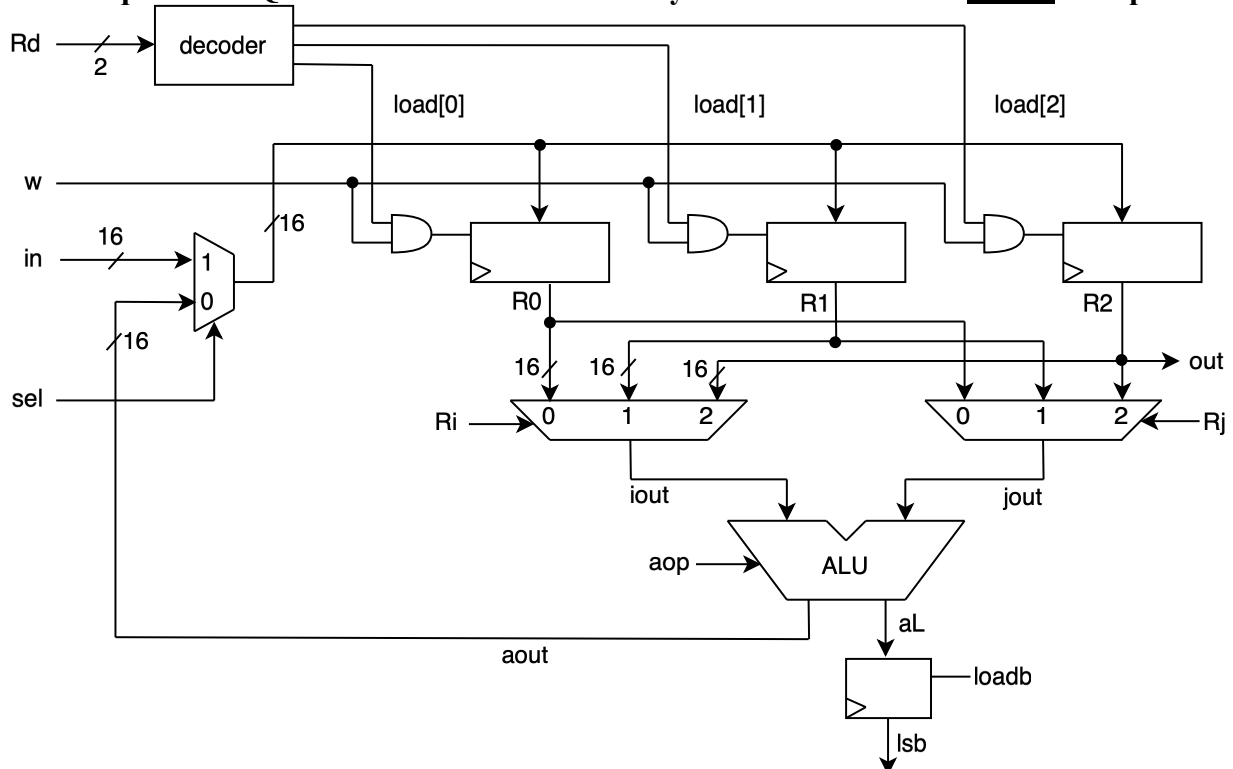

CPEN 211 Introduction to Microcomputers, 2024
Lab Proficiency Test #3

Question 2 [2.5 marks, part marks possible]: Create a state machine to control the datapath described in Question 1. Make a new file named “q2.sv” and include the starter code for module mult below then add **synthesizable** Verilog where says “// IMPLEMENT YOUR CONTROLLER HERE”. Your q2.sv will be autograded using a **reference (i.e., correct)** datapath module. To test mult, create a project with q1.sv and q2.sv. Do **NOT** include your datapath code in q2.sv. To avoid synthesis errors during testing use different names for other modules needed in both files.

```
module mult(clk,reset,s,op,in,out,done);
    input clk, reset, s;
    input [15:0] in;
    input [4:0] op;
    output [15:0] out;
    output done;
    wire [1:0] Rd, Ri, Rj, aop;
    wire w, loadb, sel, lsb;
    datapath DP(clk,Rd,w,in,sel,Ri,Rj,lsb,aop,loadb,out);
    // IMPLEMENT YOUR CONTROLLER HERE
endmodule
```

Using the datapath defined in Question 1 module mult implements the instructions defined in the table below. Input “op” to module mult is a 5-bit instruction encoded as in the column “Encoding”. In the column “Operation” in the table, the notation “in” refers input “in”, “N” refers to the 1-bit signal N inside datapath, and R[n] refers to the 16-bit contents of register Rn inside datapath (defined in Question 1). E.g., if i is 2'b10 then R[i] refers to the 16-bit value R2.

Marks	Assembly	Encoding (op)					Operation (may require more than one cycle)
		4	3	2	1	0	
1	MOV i	0	i		0	0	R[i] = in
0.5	LSR i	0	i		0	1	R[i] = R[i] >> 1
0.5	LSL i	0	i		1	0	R[i] = R[i] << 1
0.25	CHK i	0	i		1	1	lsb = aL ? 1 : 0
0.25	ADC i, j	1	i		j		if (lsb == 1) R[i] = R[i] + R[j]

The notation “a << b” means left shift the value “a” by “b” bit positions with zeros shifted into the least significant bit positions; “a >> b” means right shift the value “a” by “b” bit positions with zeros shifted into the most significant bit positions; and “a?b:c” has the meaning taught in class. Your controller should reset to a wait state on the next rising edge of “clk” if “reset” is 1. In the wait state output “done” should be set to 1. The input “s” is initially 0 but will be set to 1 to indicate the values of “in” and “op” are valid and that your module should begin executing the instruction specified by “op”. When “s” is set to 1 the inputs “in” and “op” will stay the same until your circuit sets “done” to 1. Your controller should stay in the wait state until the input “s” is 1 and there is a rising edge of “clk”. While executing an instruction, output “done” should be set to 0 until the instruction has finished and “done” must be 0 for at least one cycle of clk (i.e., the length of time between two rising edges of clk). When your controller has finished executing an instruction it must return to the wait state. tb_check_q2 inside tb.v (from URL in Question 1) should print “INTERFACE OK” and **generate no ModelSim warnings**. The testbench tb_mult found in tb.sv uses mult to multiply 6 by 7. *Hint: Tor’s solution for q2.sv is 33 lines long.*