

CPEN 211 Introduction to Microcomputers, 2021
Lab Proficiency Test #1

Question 1 [3 marks]: Create a file named “q1.v” and inside it write **synthesizable** Verilog that implements the Moore finite state machine illustrated in the figure below. Like the examples in class, state transitions occur on the rising edge of input “clk” and the reset is synchronous (occurs on the rising edge of clk) and is active high (reset equal to 1'b1 means reset). Bits on the left are most significant (have higher index value). Transitions from a state to itself are not explicitly shown. The condition for an unlabeled edge is always true. The input “in” is 2-bits wide. The output “out” is 3-bits wide. The output for each state is shown in square brackets. For example, when in state A, out should be 000, and if in is 01, then the next state should be B. The autograder used to mark your answer will assume your top-level module is called “top_module” with inputs “clk”, “reset” and “in”, output “out” declared as follows:

```
module top_module(clk,reset,in,out);
    input clk, reset;
    input [1:0] in;
    output [2:0] out;
```

Your q1.v file **must** include definitions for any modules instantiated inside top_module (even those from the slides or textbook). You should test your code and you can include testbench modules in q1.v, but testbench modules inside q1.v will be ignored by the autograder. **Upload your Verilog file named “q1.v” by attaching it as your solution to Question 1 under “Lab Proficiency Test #1” on Canvas before 6:45 pm.** In case your computer’s time differs from Canvas submit early and resubmit as needed. Marks will be deducted for submissions made after 6:45 pm and no submissions will be accepted after 6:50 pm (**emailed submissions will not be accepted**). Do **NOT** “zip” your submission. The file you upload for this question **must** be called “q1.v” or the autograder script will not mark it.

Your solution for Question 1 will get zero if any of the following are true:

1. Your **last** “Lab Proficiency Test #1” attempt on Canvas does not include “q1.v”,
2. Your q1.v file does not compile using ModelSim (e.g., due to syntax errors),
3. Your q1.v file does not contain a module called top_module with inputs/outputs as above,
4. Your top_module cannot be simulated (e.g., due to missing module definitions in q1.v),
5. The Verilog used by your top_module is not synthesizable by Quartus.
6. The Verilog used by your top_module has any inferred latches.
7. Your top_module output “out” does not exactly match the output of the state machine below for some sequence of values for inputs “clk”, “reset” and “in”.

 


Figure 1